

## W7. Control Unit Construction

---

### One Hot Encoding for the implementation of FSMs

#### 1. Laboratory objective

*Implementation of control units using One Hot Encoding*

#### 2. Theoretical Background

##### 2.1 One Hot encoding

**One Hot Encoding** for an FSM having  $n$  states uses  $n$  storage elements. Each storage item is associated with a state. Consequently, at each time point, only one of the  $n$  storage elements has the output active. The FSM implemented using One Hot encoding uses an increased number of storage elements, but benefits from a direct implementation and easy troubleshooting.


##### 2.2.1 Divide-by-N Counter

A divide-by- $n$  counter divides the frequency of the input clock signal by the factor  $n$  and is built around a modulo- $n$  counter. A modulo- $n$  counter is composed of:

- A register on  $r$  bits (  $r = \lceil \log_2 n \rceil$  )
- A component for incrementing the contents of the register
- A synchronous **clear** signal activates when its contents reach  $n-1$ .

The divide-by- $n$  counter has 2 synchronous inputs: **c\_up**, to activate the counting sequence and **clr**, to delete the register's content. Also, the divide-by- $n$  counter has the output on 1-bit **dclk** (divided clock), activated once every  $n$  clock cycles.
 
## 2.2.2 State transition diagram: divide-by-5 counter



The design uses 5 flip-flops type **D**, **FF0**, **FF1**, **FF2**, **FF3**, and **FF4**, with the inputs **Di** and the outputs **Qi**, associated with the 5 states **S0**, **S1**, **S2**, **S3**, and **S4** (as illustrated in the diagram above). At any time only one of the 5 flip-flops is active, with the **Qi** output equal to 1. The current status is indicated by the flip-flop with the active output. If **Q1** is active the current state is **S1**, if **Q4** is 1 then **S4** is the current state, and so on. The boolean equations that activate the **Si** states are connected to the **Di** inputs. The design of the **FSM** unit is reduced to writing these equations. Example: From the transition diagram, the next state is **S1** if the current state is **S0**, **c\_up** is 1 and **clr** is 0, or the current state is **S1** and neither **c\_up** nor **clr** is 1. So we can write accordingly:

$$D_1 = Q_0 \cdot c\_up \cdot \overline{clr} + Q_1 \cdot (\overline{clr} \cdot \overline{c\_up})$$

The other 4 D inputs are built similarly.

### 3. Divide-by-5 counter: One Hot encoding and Verilog code

#### Laboratory Task

Complete the template below with the missing Boolean equations deduced from the state transition diagram on page 2:

```

1  module d5cntr(
2      input clk,
3      input rst_b, //asynch
4      input clr,
5      input c_up,
6      output dclk
7  );

9      //vector of inputs D for all 5 flip flops (FFs); din[0] is input to FF0;
10     //FF0 indicates whether the current state is S0 or not
11     reg [4:0] din;
12     //next value for all 5 FFs; corresponds to the next state
13     wire [4:0] din_nxt;

15     //boolean equation setting the next state to S1:
16     //      D1      =      Q0      * c_up * (~clr) +      Q1      * (~c_up) * (~clr)
17     assign din_nxt[1] = (din[0] & c_up & (~clr)) | (din[1] & (~c_up) & (~clr));
18     //boolean equations for activating states S0, S2, S3, S4
19     //...

21     //output activation
22     assign dclk = din[0]; //dclk activated once every 5 clock cycles;
23     //one can choose any state to activate the output

25     //update the current states vector
26     always @ (posedge clk, negedge rst_b)
27         if (! rst_b) din <= 5'd1; //set current state to S0 by
28         //setting FF0 and clearing all other FFs
29         else din <= din_nxt;
30 endmodule

```

### 4. References

[Vlad12] M. Vlăduțiu, “Computer Arithmetic: Algorithms and Hardware Implementations” Springer, 2012.