


Week 3 - Verilog Module Instantiations

Combinational Always Blocks and Instances in Verilog

P.3.1 Design, using a combinational always block, a 2-to-1 multiplexer having 3 inputs: **s**, **d0**, and **d1**, and having one output, denoted by **o**.


Solution:
 
```
module mux_2_to_1 (  
    input s,  
    input d0,  
    input d1,  
    output reg o  
);  
always @(*) begin  
    if (s) o = d1;  
    else o = d0  
end  
endmodule
```



P.3.2 Consider the architecture of a 2-to-4 line decoder, named **dec_2x4**. The decoder has a 2-bit selection line **s**, a 4-bit declared **y** output, active on 1, and an enable line (**e**) which when set to 1 allows the decoder unit to operate. Construct the module using a combinational always block.

Solution:

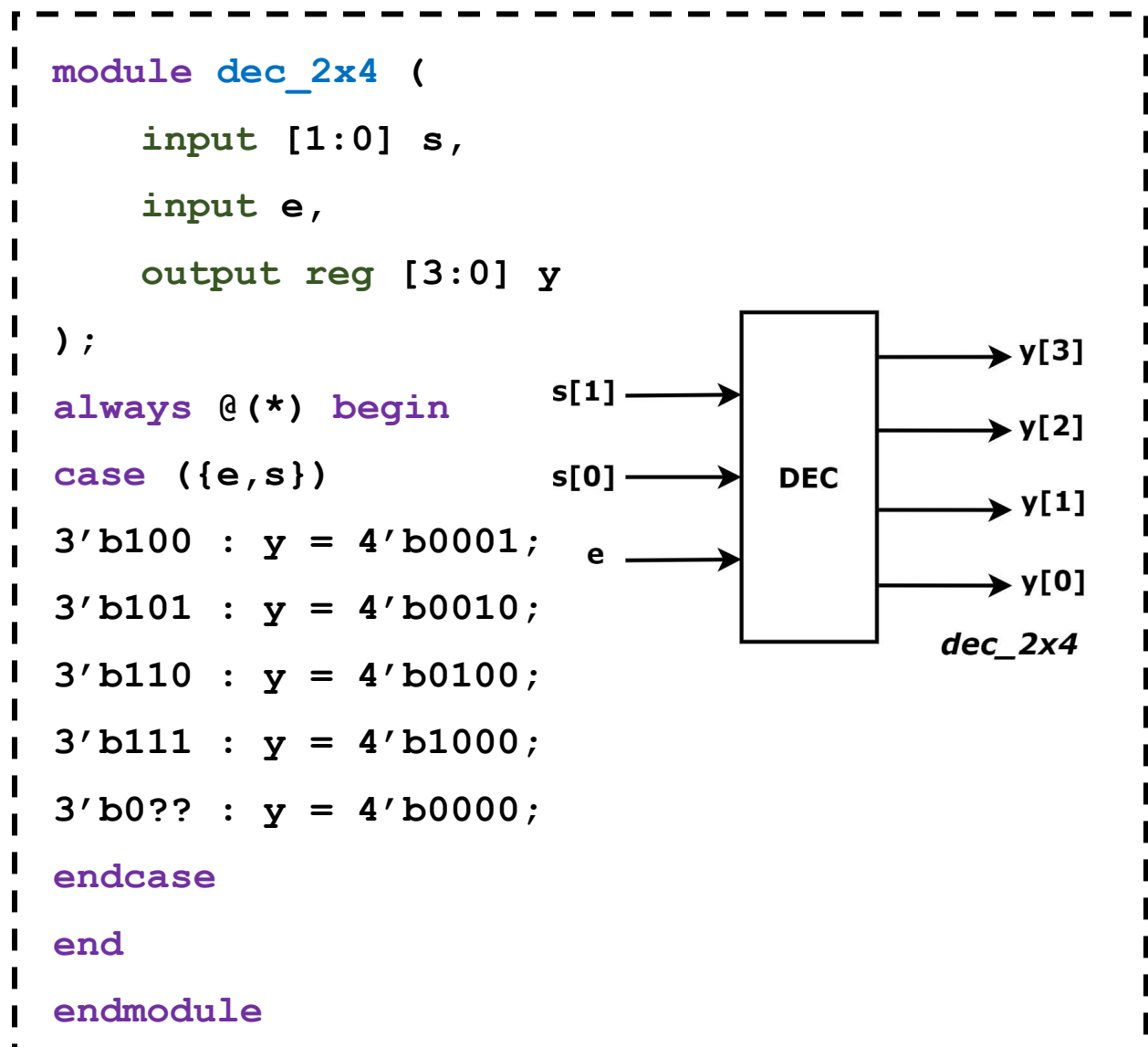

P.3.3 Design, using Verilog, an 8-to-1 multiplexer with 2 inputs: *s* on 3 bits, *d* on 8 bits, and an output *o*. Construct the hierarchical design of the multiplexer, using instances of the *mux_1s_1b* module implemented in **P.3.1**.

Solution:

```
module mux_8_to_1 (
    input [2:0] s,
    input [7:0] d,
    output o
);
    wire w1,w2,w3,w4,w5,w6;
    // Layer 1
    mux_1s_1b m1 (
        .d1(d[7]), .d0(d[6]), .s(s[0]), .o(w1) );
    mux_1s_1b m2 (
        .d1(d[5]), .d0(d[4]), .s(s[0]), .o(w2) );
```

```

mux_1s_1b m3 (
.d1(d[3]), .d0(d[2]), .s(s[0]), .o(w3) );
mux_1s_1b m4 (
.d1(d[1]), .d0(d[0]), .s(s[0]), .o(w4) );
// Layer 2
mux_1s_1b m5 (
.d1(w1), .d0(w2), .s(s[1]), .o(w5) );
mux_1s_1b m6 (
.d1(w3), .d0(w4), .s(s[1]), .o(w6) );
// Layer 3
mux_1s_1b m7 (
.d1(w5), .d0(w6), .s(s[2]), .o(o) );
endmodule

```

P.3.4 Design, using Verilog, an 8-to-1 multiplexer with 2 inputs: *s* on 3 bits, *d* on 8 bits, and one output *o*. Implement the hierarchical design of the multiplexer using instances of the *mux_1s_1b* and *mux_2s_1b* modules, respectively.


Solution:

```
module mux_2s_1b (  
    input [1:0] s,  
    input [3:0] d,  
    output o  
);  
assign o = s[1] ? (s[0]?d[3]:d[2]):(s[0]?d[1]:d[0]);  
endmodule
```

```
module mux_8_to_1 (  
    input [2:0] s,  
    input [7:0] d,  
    output o    );  
wire w1,w2;  
// Layer 1  
mux_2s_1b m1 (  
    .d(d[7:4]), .s(s[1:0]), .o(w1) );  
mux_2s_1b m2 (  
    .d(d[3:0]), .s(s[1:0]), .o(w2) );  
// Layer 2  
mux_1s_1b m3 (  
    .d1(w1), .d0(w2), .s(s[2]), .o(o) );  
endmodule
```

Annexes

P.3.3 Figure

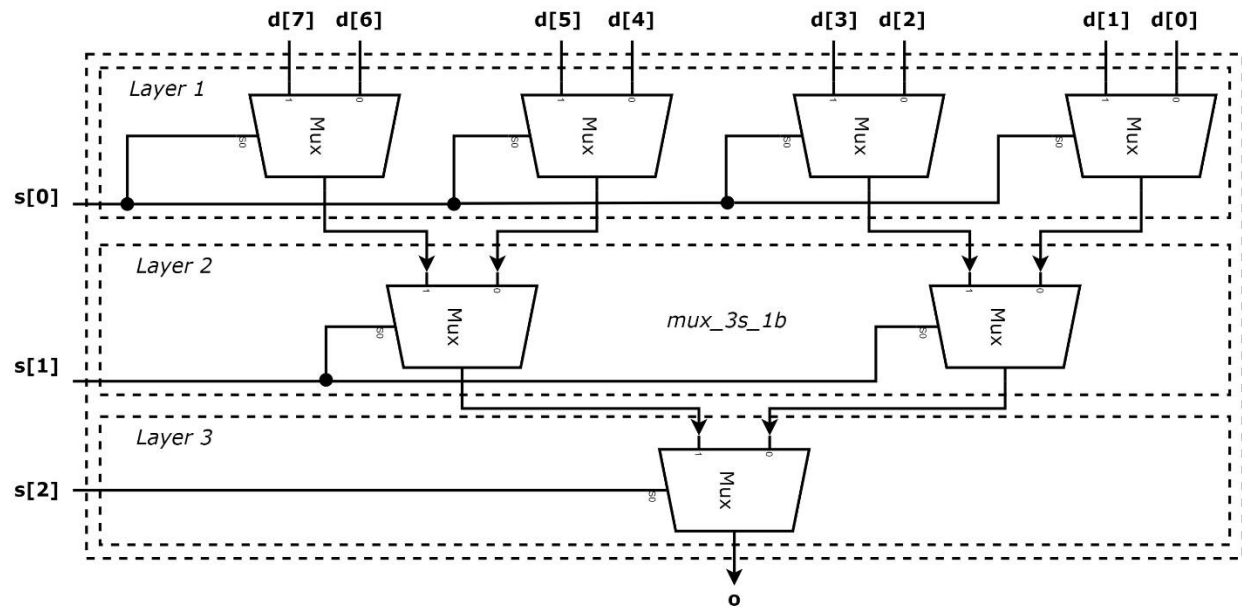

P.3.4 Figure

