

## W3. Designing hierarchical architectures

---

### Instantiating modules in Verilog language

#### 1. Objectives

O1. Learning the technique of instantiating a module in Verilog language

O2. Implementation of a decoder device in Verilog HDL

O3. Building a hierarchical design

#### 2. Theoretical Background

##### 2.1 Hierarchical Design

We will emphasize that a hierarchical design::

- facilitates the design of complex architectures
- encourages the reuse of the designed design

##### 2.1.1 Instance

**The instance** can be defined as a module used as a component in a more comprehensive module.

An instance has:

- A **module**: provides the definition for the instance.
- A **recipient**: the module in which the instance is created.

The procedure by which we create a new instance is called **instantiation**.

An instance is built by the following elements:

- the module to be instantiated, followed by
- the name of the instance (which differs from other instances of the same module), followed by a list of ports.

The list of ports specifies which signals from the container are linked to the instance ports.

A port connection is defined most simply:

`.<module_port>(<container_signal>),` in which:

- **module\_port** is a port of the instantiated module.
- **container\_signal** is an internal signal or a container port.

## 2.1.2 The architecture of a 4-to-1 multiplexer


### Exercise:

Build a 4-to-1 multiplexer by using instances of 2-to-1 multiplexers.

### Solution:

The architecture of a 4-to-1 multiplexer using three 2-to-1 multiplexer modules is illustrated below. The data input, **d**, is on 4 lines and the selection line **s**, on 2 bits, propagates 1 bit from input **d** to output **o**.

For example, if **s** = (1,0), the line **d** [2] is propagated to **o**.

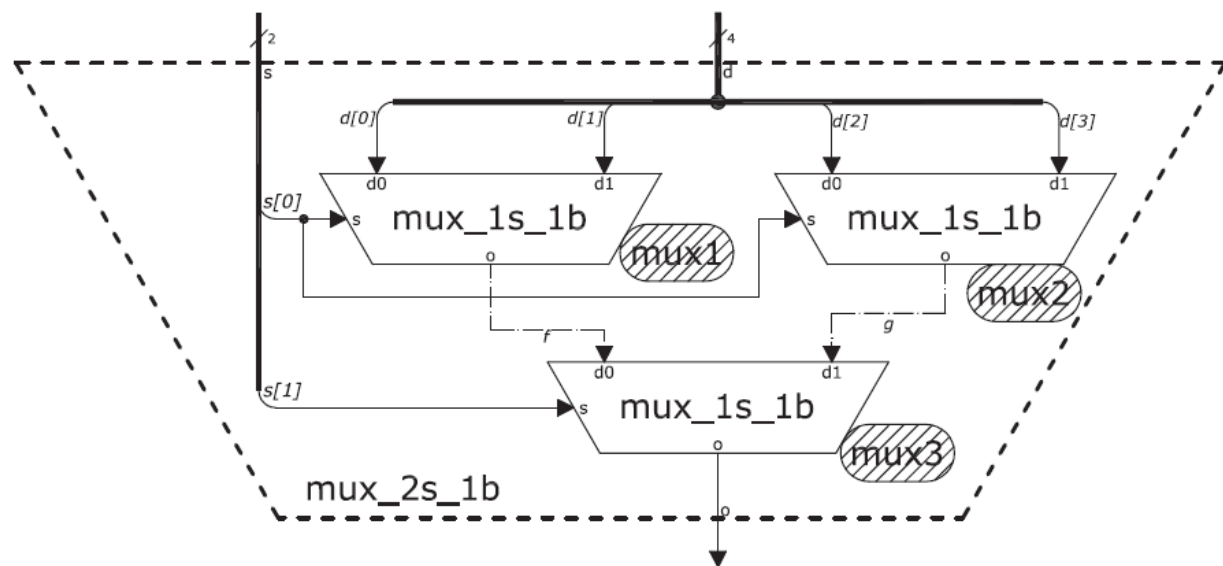

**Fig. 1 – Hierarchical Design of a 4-to-1 multiplexer**

The Verilog code that implements the architecture of a 4-to-1 multiplexer is presented below:

```

module mux_1s_1b (
    input [3:0] d,
    input [1:0] s,
    output o
);

    mux_1s_1b mux2 (
        .d0(d[2]) ,
        .d1(d[3]) ,
        .s(s[0]) ,
        .o(g)
    );

    wire f;
    wire g;

    mux_1s_1b mux3 (
        mux_1s_1b mux1 (
            .d0(f) ,
            .d0(d[0]) ,
            .d1(d[1]) ,
            .s(s[0]) ,
            .o(f)
        ),
        .d1(g) ,
        .s(s[1]) ,
        .o(o)
    );

endmodule

```

By carefully analyzing the first instance created in the 4-to-1 multiplexer code, we can observe the components of an instantiation:

- the module to be instantiated is **mux\_1s\_1b** (must be the name of an existing Verilog module)
- the instance name is **mux1** (must be a valid Verilog name)
- list of connection ports, positioned between **round brackets** (more details below on the current page)

```

mux_1s_1b mux1 (
.d0(d[0]),
.d1(d[1]),
.s(s[0]),
.o(f)
);

```

 


Fig. 2 – Module mux1 Instantiation

The elements of the first connection port are::

- d0** - port of the mux\_1s\_1b module to be associated with
- d[0]** - signal inside the container mux\_2s\_1 (d[0] is a port of a container, thus a signal in the container) to which d0 is connected.

Internal **wire** type links connect internal instances:

- connects an exit of the instance to an input of another instance.
- must be declared in the module container as **wire** elements

 


Fig. 3 – Declaring the internal physical wires of the architecture `mux_2s_1b`

**Important:** When connecting a wire to a port, their widths (dimensions) must be identical!

If the two ports to be connected have different sizes, choose a width of one of them for the size of the physical wire to be connected. To connect the wire to the desired port:

- if the physical wire has fewer lines and the other port is an output, some of the output lines will remain unconnected
- if the physical wire has fewer lines and the port to which it connects is an input, use the concatenation operation to provide the required input lines  
ex: `.x({4'd0, data}),)`
- if the wire has multiple lines and the opposite port is an input, use part-select to provide only the required input lines  
ex: `.s(addr[15:14]),)`
- if the wire has multiple lines and the port it connects to is an output, use part-select to provide the required output lines  
ex: `.z(next_addr[7:0]),)`

 


Fig. 4 – Connecting inputs and outputs to declared physical wires

The Verilog code illustrated above:

- connects the output o of **mux1** to wire **f** (see left)
- connects the **d0** input of **mux3** to wire **f** (see right side)