

# W5. Design of reusable modules

---

## Implementing parameterized modules in Verilog

### 1. Objectives

- O1. Learning how to separate *datapath* and *control path* instances
- O2. Introduction of the concept of reusable mode
- O3. Learn how to write parameterized modules

### 2. Theoretical Background

#### Datapath

The **Datapath** instance consists of elements that process the data: no decisions are made. Typical components here are:

- multiplexers (MUX)
- registers (REG)
- arithmetic-logical units (ALU)

In addition, the Datapath instance builds common buses using three-state logic gates.

#### Control path

The **Control path** involves decision making and is described in terms of machines with states.

**Note:** Components with validation states (such as registers, counters) can also be part of the datapath.

## Reusable Modules

**Reusable modules** are defined as modules which integrate **parameters**, that can be redefined. In the Verilog 2001 standard, the parameters of the module are specified in a dedicated section, marked by the symbols # (s, i). The code below describes a parallel register, with parameterizable width (number of bits) and initialization vector (contents of the register after reset).

```
module rgst #(
    parameter w = 8, //register width parameter, with default value 8
    parameter iv = {w{1'b0}} //initialization vector parameter
)(
    input clk , //clock signal
    input rst_b , //asynchronous reset; active on low
    input [w-1:0] d , //input data on w bits
    input ld , // synchronous load; active on high
    input clr , // synchronous clear; active on high
    output reg [w-1:0] q //the contents of the register, on w bits
);
always @ ( posedge clk, negedge rst_b )
begin
    if (! rst_b)
        q <= iv; //setting the content to the initialization value
    else if (clr)
        q <= iv; //setting the content to the initialization value
    else if ( ld )
        q <= d;
end
endmodule
```

### 3. Applications

**Exercise:** Build a  $4 \times 8$  register file.


**Solution:** An  $M \times N$  **register file** is a storage element organized as a vector of  $M$  registers, each register having  $N$  bits. Allows you to simultaneously read an internal register and write an internal register (possibly the same).

The interface of a register file includes the following connections:

- An  $N$ -bit data entry for writing internal registers ( $wr\_data$ )
- $N$ -bit data output for reading internal registers ( $rd\_data$ )
- An input address, for selecting the register to be written ( $wr\_addr$ )
- An output address, for selecting the register to be read ( $rd\_addr$ )
- Write validation signal ( $wr\_e$ )
- Read validation signal ( $rd\_e$ )

The validation lines for the write/read port are optional,  $M$  generally takes the form of  $2^k$ : the input/output addresses use  $k$  bits.

The interface of a  $4 \times N$  register file is shown below:

 

**Fig. 1 – Structure of a register file**

For the presented scenario, the interface consists of:

- Writing port ( $wr\_data$ ,  $wr\_addr$ ,  $wr\_e$ )
- Read port ( $rd\_data$ ,  $rd\_addr$ ,  $rd\_e$ )
- The clock signal ( $clk$ )
- The reset signal ( $rst\_b$ )

A register file  $4 \times 8$  without validation line on the output:


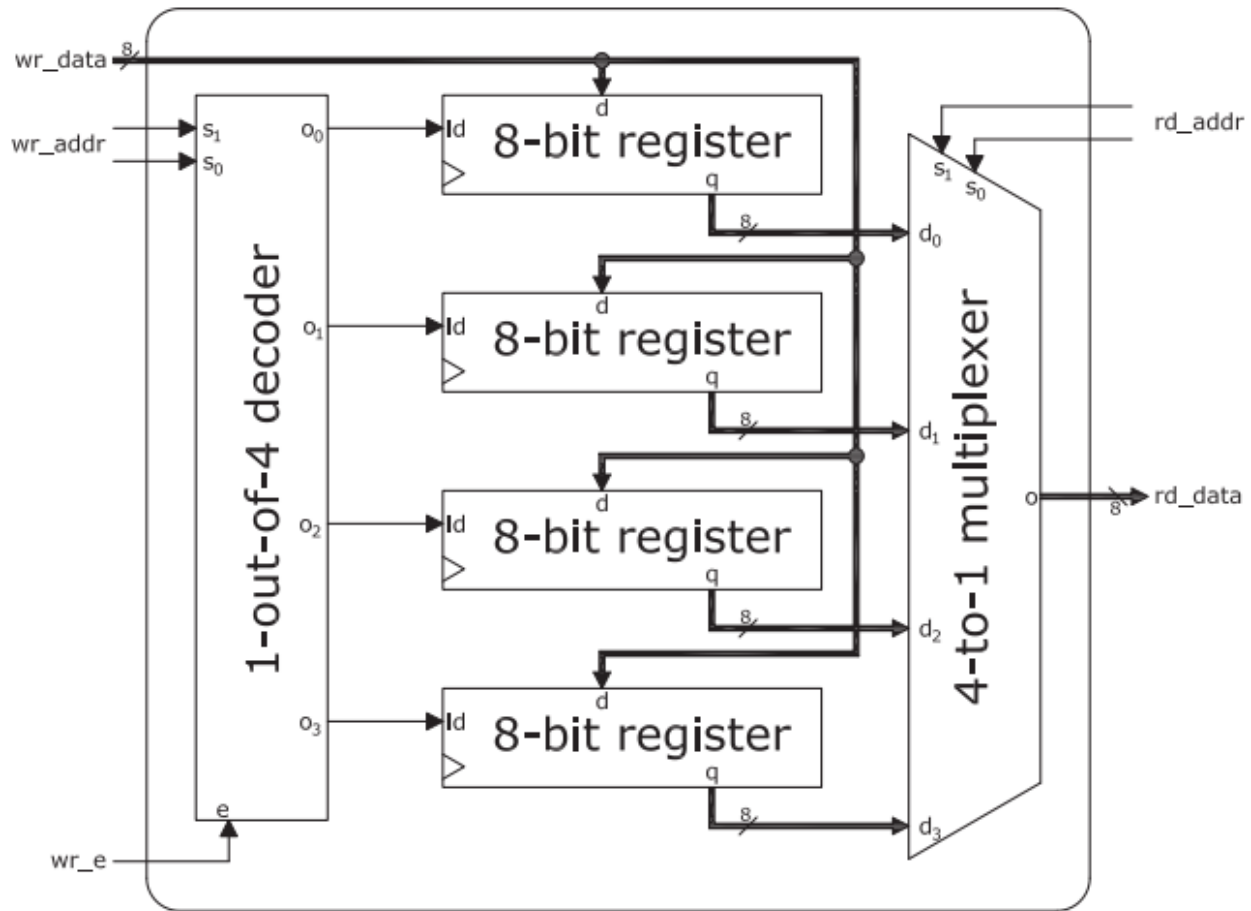


Fig. 2 – Architecture of a register file

**Note:** The *clock* and *reset* lines have been omitted for clarity.

### Three-state gates

 

It is used to connect several components on a common line or bus.

Output  $o$  is set to  $i$  when the validation line is active, and on **high impedance** in the opposite scenario. An output set to high impedance (symbolized **z**, in Verilog) allows another component connected to the same line (or bus) to set the line value.


The code fragment below exemplifies the control of a signal to high impedance, using a control line *e*:

```
wire [15:0] data, data_hiz ;
assign data_hiz = (e) ? data : 16'bz
```

Since the high impedance symbol *z* represents the most significant bit of the constant on line 2, it will extend by 16 bits *z*.

### Construction of a multiplexer using three-state gates

A 4-to-1 *n*-bit multiplexer is implemented using three-state logic gates:

 

**Fig. 3 – The architecture of a multiplexer implemented with trivalent gates and a decoder**

#### Observation:

In general, explicitly redefining the parameters of a module in Verilog 2001 uses the following format:

```
module-name # ( .parameter-name(value) , ... )
    instance_name ( .port-name(signal) , ... )
```

The code on the next page instantiates a 16-bit register, with an initialization value set to 0.

```
rgst #(
    .w(16)
) registru1 (
    .clk(clk), ...
);
```

Another code below instantiates a 4-bit register with an initialization value set to 15.

```
rgst #(
    .w(4)
    .iv(4'd15)
) registru2 (
    .clk(clk), ...
);
```