 


Laboratory Week 10 CA

Building multiple instances in Verilog language

E.10.1 Design the architecture of a **BCD8421** to **E3** converter for **k**-digit numbers, using **k** instances of a 4-bit adder, called **add4b**. Implement the design in Verilog language, using a **generate** construct.

The complete architecture is given below:




E.10.2 Design the architecture of a Register File 16 x 32, as illustrated below. The **reg_fl** module will receive 32-bit data packets at the input and its output will deliver a

512-bit data block by concatenating all the outputs of the internal registers of the architecture.

a) Implement the *dec_4s* module, using Verilog language.

b) Implement the parameterized *rgst* module, using Verilog language.

 c) Construct the *reg_fl* architecture, using the multiple instantiation method.



a) Decoder module

```
module dec_4s ( input [3:0] s,  
                input e,  
                output reg [15:0] o );  
  
always @(*) begin  
    case ({e, s})  
        5'b10000: o = {15'b0, 1'b1};  
        5'b10001: o = {14'b0, 1'b1, 1'b0};  
        5'b10010: o = {13'b0, 1'b1, 2'b0};  
        5'b10011: o = {12'b0, 1'b1, 3'b0};  
        5'b10100: o = {11'b0, 1'b1, 4'b0};  
        5'b10101: o = {10'b0, 1'b1, 5'b0};  
        5'b10110: o = {9'b0, 1'b1, 6'b0};  
        5'b10111: o = {8'b0, 1'b1, 7'b0};  
        5'b11000: o = {7'b0, 1'b1, 8'b0};  
        5'b11001: o = {6'b0, 1'b1, 9'b0};  
        5'b11010: o = {5'b0, 1'b1, 10'b0};  
        5'b11011: o = {4'b0, 1'b1, 11'b0};  
        5'b11100: o = {3'b0, 1'b1, 12'b0};  
        5'b11101: o = {2'b0, 1'b1, 13'b0};  
        5'b11110: o = {1'b0, 1'b1, 14'b0};  
        5'b11111: o = {1'b1, 15'b0};  
        5'b0????: o = 16'b0;  
    endcase  
end  
endmodule
```

b) Parameterized register module

```
module rgst # (  
    parameter w = 8,  
    parameter iv = {w{1'b0}}  
)(  
    input clk,  
    input rst_b,  
    input [w-1:0] d,  
    input ld,  
    input clr,  
    output reg [w-1:0] q  
);  
  
always @ ( posedge clk, negedge rst_b)  
    if(! rst_b)  
        q <= iv;  
    else if(clr)  
        q <= iv;  
    else if(ld)  
        q <= d;  
  
endmodule
```

c) Register File module with generate construct

```
module reg_fl( input clk, rst_b,  
              input [31:0] d,  
              input [3:0] s,  
              input we,  
              output [511:0] q );  
wire [15:0] r_ld;  
dec_4x16 u_dec ( .s(s), .e(we), .o(r_ld) );  
generate  
    genvar i;  
    for( i=0; i<16; i=i+1 )  
    begin: arr  
        rgst #(  
            .w(32)  
        ) u_rgst(  
            .clk(clk),  
            .rst_b(rst_b),  
            .d(d),  
            .clr(1'd0),  
            .ld(r_ld[i]),  
            .q(q[i*32+31 : i*32])  
        );  
    end  
endgenerate  
endmodule
```