 


Week 2 - Introduction – Proposed Problems

Verilog Modules and Operators


P.2.1 Design, using Verilog, a 2-to-1 multiplexer on 2 bits, having 3 inputs: *s*, *d0*, and *d1*, and having one output, denoted by *o*.



Solution:

```
module mux_1s_2b (
    input s,
    input [1:0] d0,
    input [1:0] d1,
    output [1:0] o
);
    assign o = s ? d1:d0;
endmodule
```

 
P.2.2 Design, using Verilog, a multiplexer on 4 bits, with 2 inputs: *s* and *d*, and one output, *o*. The multiplexer selects either the most significant half of the input *d* or the least significant half of the same input, if *s* has the value 1 or 0, respectively.



Solution:

```
module mux_sel (  
    input s,  
    input [3:0] d,  
    output [1:0] o  
);  
    assign o = s ? d[3:2]:d[1:0];  
endmodule
```

 P.2.3 Design, using Verilog, a module that attaches, depending on an input **swch**, 3 bits of 1 on the most significant positions of the input **i** if **swch** is 1, or 3 bits of 0 on the least significant positions if **swch** is 0. The input **i** is declared as 5 bits, and the module's output is **o**.



Solution:

```
module switch (  
    input swch,  
    input [4:0] i,  
    output [7:0] o  
);  
    assign o = swch ? {3'd7,i}:{i,3'd0};  
endmodule
```

P.2.4 Build a module for reversing the order of the bits of a 5-bit value received at the input.



Solution:

```
module reverse_5b (  
    input [4:0] i,  
    output[4:0] o  
);  
assign o = {i[0],i[1],i[2],i[3],i[4]};  
endmodule
```

P.2.5 Design, using Verilog, a module that separates the integer part from the fractional part of a number connected to the module's input. A 5-bit number is allocated for the ***integer part*** of the input, and a 3-bit number is reserved for the ***fractional part***.



Solution:

```
module separator_8b (  
    input [7:0] i,  
    output [4:0] in, // integer part  
    output [2:0] fr // fractional part  
);  
assign in = i[7:3];  
assign fr = i[2:0];  
endmodule
```

P.2.6 Implement, using Verilog language, a module for testing the zero value of an 8-bit number represented in Sign-Magnitude without using the relational operator `==`.



Solution:

```
module zero_tester (  
    input [7:0] in,  
    output zero  
);  
assign zero = | in[6:0];  
endmodule
```

P.2.7 Implement, using Verilog language, a module that attaches a parity bit to a 7-bit input. The 8-bit output will have the parity bit placed in the least significant position.



Solution:

```
module parity_bit (  
    input [6:0] in,  
    output[7:0] out  
);  
    assign out = {in, ^in};  
endmodule
```

P.2.8 Design, using Verilog, a module to check the parity generated by the previous module. The module will have an 8-bit input *i*, a 7-bit output *o* representing the most significant 7 bits of the input, and an active output *err* indicating if the parity bit was calculated incorrectly.



Solution:

```
module parity_checker (  
    input [7:0] i,  
    output[6:0] o,  
    output err  
);  
    assign out = i[7:1];  
    assign err = ^i;  
endmodule
```


P.2.9 Implement, using Verilog, a module for converting 8-bit numbers from Sign-Magnitude to One's Complement.



Solution:

```
module converter_8b (  
    input [7:0] i,  
    output [7:0] o  
);  
assign o = i[7] ? {i[7], ~i[6:0]} : i;  
endmodule
```

P.2.10 Build, using Verilog, a module for detecting multiples of 3 connected to its input. The input *i* is declared on 4 bits, and the module's name is ***mul_3***.



Solution:

```
module mul_3 (  
    input [3:0] i,  
    output o  
);  
assign o = (i%3==0) ? 1 : 0;  
endmodule
```

P.2.11 Design a module for comparing 2 numbers, **x** and **y**, each on 1 bit. The module has the output **eq** active if the numbers **x** and **y** are equal, the output **le** active if **x** is less than **y**, and the output **gt** active if **x** is greater than **y**.



Solution:

```
module comparator_1b (  
    input x,y,  
    output eq,le,gt  
);  
assign eq = x ~^ y;  
assign le = x & (~y);  
assign gt = (~x) & y;  
endmodule
```

P.2.12 Design, using Verilog, a module that displays the most significant decimal digit of an unsigned 4-bit input.



Solution:

```
module msd (  
    input [3:0] i,  
    output [3:0] o  
);  
assign o = i > 4'd9 ? 4'd1 : i;  
endmodule
```