

## Week 4 – Using always and initial blocks

### Using sequential always blocks

**P.4.1** Implement, using Verilog, a module for a **D**-type flip-flop (flip-flop) circuit having an asynchronous, active-low **reset line**. Use a **sequential always block** for the behavioral description of the circuit.

**Solution:**

```
module dff_ar (  
    input d,  
    input clk,  
    input rst_b,  
    output reg q
```

```
);
```


```
always @(posedge clk, negedge rst_b) begin
```

```
if (!rst_b) q <= 1'b0;
```


```
else q <= d;
```

```
end
```

```
endmodule
```

 

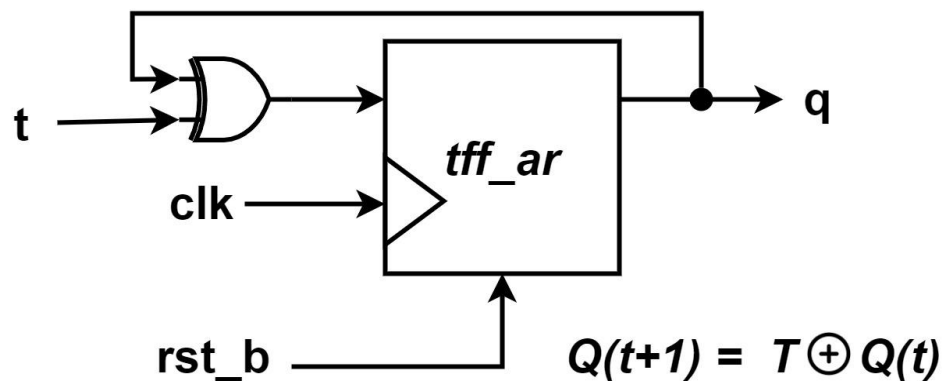**P.4.2** Implement, using Verilog, a module for a  $T$ -type flip-flop circuit, characterized by the relationship:  $Q(t+1) = T \oplus Q(t)$  and having the asynchronous **reset line**, active low. Use a **sequential always block** to describe the circuit in the statement.



**Solution:**


```

module tff_ar (
    input t, clk, rst_b,
    output reg q
);
    always @(posedge clk, negedge rst_b) begin
        if (!rst_b) q <= 1'b0;
        else q <= t ^ q;
    end
endmodule

```

**P.4.3** Design, using Verilog, the sequential circuit architecture shown below using:

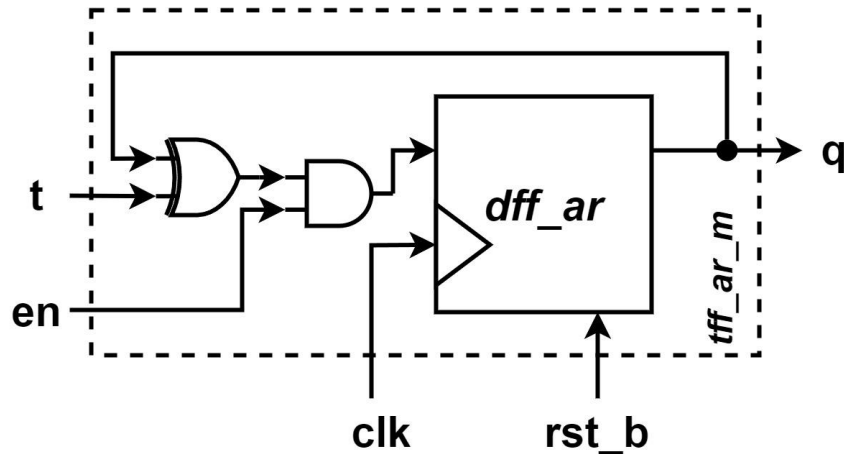- a ***dff\_ar*** instance for the modified variant in the figure.
- a ***sequential always block***.



**Solution: a)**

```
module tff_ar_mod (  
    input t, en, clk, rst_b,  
    output q  
);  
    wire w1;  
    assign w1 = (t^q) & en;  
  
    dff_ar t1 (.d(w1), .clk(clk), .rst_b(rst_b), .q(q) );  
endmodule
```

### ***Solution: b)***

```
module tff_ar_mod (  
    input t, en, clk, rst_b,  
    output reg q  
);  
always @(posedge clk, negedge rst_b) begin  
    if ((!rst_b) || (!en)) q <= 1'b0;  
    else if (en) q <= t ^ q;  
end  
endmodule
```

**P.4.4** Design, using Verilog, a 2-bit parallel load register with a clock (***clk***), asynchronous reset line (***rst***), a load line (***ld***), a 2-bit ***d*** input, and a 2-bit output denoted by ***q***.

a) Draw the detailed architecture of the 2-bit parallel load register, ***reg\_parl\_2b***.

b) Construct, by instantiation, the architecture designed in subpoint ***a***).


```

module reg_par1_2b    (
    input clk, rst, ld,
    output [3:0] q    );
    wire w1,w2;

    //Layer 1
    mux_1s_1b m1 (.d1(d[1]), .d0(q[1]), .s(ld), .o(w1));
    mux_1s_1b m0 (.d1(d[0]), .d0(q[0]), .s(ld), .o(w2));
    // the mux_1s_1b module is reused from previous laboratory
    //Layer 2
    dff_ar dff1 (.d(w1), .clk(clk), .rst(rst), .q(q[1]));
    dff_ar dff0 (.d(w2), .clk(clk), .rst(rst), .q(q[0]));
endmodule

```

**P.4.4 a)**

 

**P.4.5** Design, using Verilog, a testbench for exhaustive checking of the ***mux\_1s\_1b*** module. The module's name will be ***mux\_1s\_1b\_tb***.

***Solution:***

```
module mux_1s_1b_tb (  
    output reg s,d1,d0,  
    output o  
);  
  
    // Instantiation  
mux_1s_1b DUT (.d0(d0), .d1(d1), .s(s), .o(o));  
  
    // Initial begin block  
integer i;  
initial begin  
    {s,d1,d0} = 3'b0;  
    for (i = 0; i < 8; i = i + 1)  
        # 50 {s,d1,d0} = i[2:0];  
end  
endmodule
```

**P.4.6** Design, using Verilog, a testbench for non-exhaustive checking of the *dff\_ar* module. The module's name will be *dff\_ar\_tb*. The clock signal has  $T = 20$  ps.

```
module dff_ar_tb (
    output reg d,clk,rst,
    output q
);
// Instantiation
dff_ar DUT (.d(d), .clk(clk), .rst(rst), .q(q));
initial begin // Clock signal generation
clk = 1'b0;
forever #10 clk = ~clk;
end
initial begin // Reset signal generation
rst = 1'b0;
#5 rst = 1'b'1;
#15 rst = 1'b'0;
#10 rst = 1'b1;
initial begin // Data signal generation
d = 1'b0;
#10 d = 1'b'1;
#15 d = 1'b'0;
#10 d = 1'b1;
end
endmodule
```