 


## Week 5 – Design of reusable modules


### Parameterized modules in Verilog
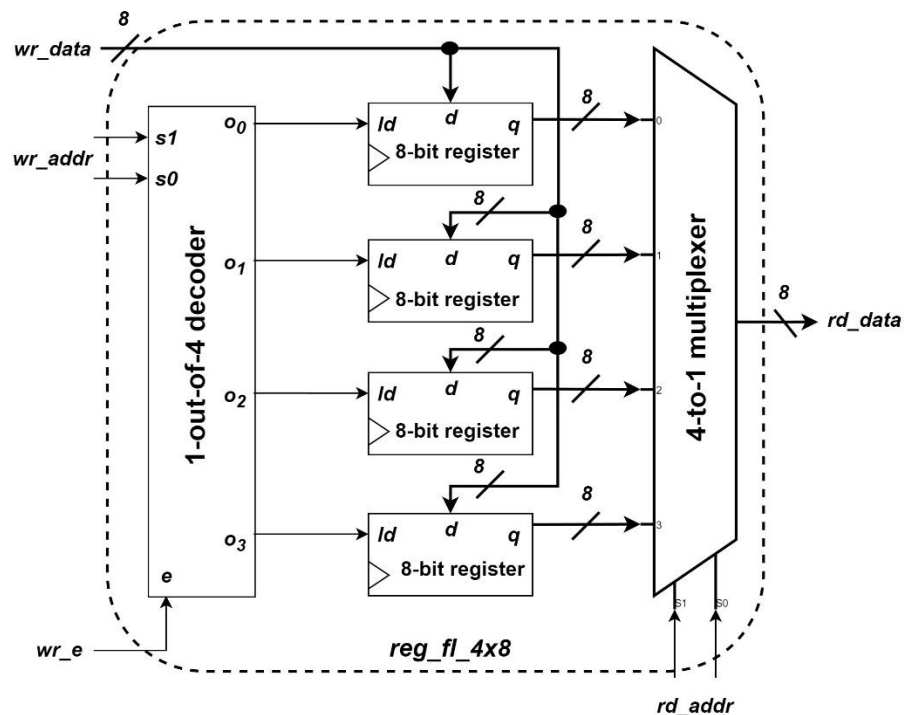
#### The Datapath

Consider the architecture of a Register File, denoted as *reg\_fl*, with the ports *wr\_data* and *rd\_data* on *n* bits, the *wr\_addr* and *rd\_addr* inputs on 2 bits, respectively the 1-bit signals *ld*, *clr*, *rst*, and *clk*. The module's graphical representation is illustrated below:



The detailed architecture of the Register File is provided as follows:



**P.5.1.** Design, using Verilog language, the decoder module depicted on the previous page, which has a 2-bit selection line (**s**), one enable line (**e**) on 1-bit, and an output on 4 bits, denoted by **o**. The module's name will be **dec\_2x4**.

- Draw the truth table of the **1-out-of-4 decoder** module.
- Implement the module using a **continuous assignment** command.
- Construct the same module using a **combinational always** block with **case statement**.

**Solution:**

**a)**

<b>Enable</b>	<b>Selection</b>		<b>Output</b>			
<b>e</b>	<b>s[1]</b>	<b>s[0]</b>	<b>o[3]</b>	<b>o[2]</b>	<b>o[1]</b>	<b>o[0]</b>
1	0	0	0	0	0	<b>1</b>
1	0	1	0	0	<b>1</b>	0
1	1	0	0	<b>1</b>	0	0
1	1	1	<b>1</b>	0	0	0
0	d	d	0	0	0	0

**b)**

```

module dec_2x4 (
    input [1:0] s,
    input e,
    output [3:0] o
);
    assign o[0] = e & (~s[1]) & (~s[0]);
    assign o[1] = e & (~s[1] & s[0]);
    assign o[2] = e & s[1] & (~s[0]);
    assign o[3] = e & s[1] & s[0];
endmodule

```


c)

```

module dec_2x4 (
    input [1:0] s,
    input e,
    output reg [3:0] o
);
always @ (*) begin
    case {e,s}
        3'b100 : o = 4'b0001;
        3'b101 : o = 4'b0010;
        3'b110 : o = 4'b0100;
        3'b111 : o = 4'b1000;
        3'b0?? : o = 4'b0000;
    encase
end
endmodule

```

 **P.5.2.** Design, using Verilog language, a **testbench** for non-exhaustive checking of the **dec\_2x4** module implemented in **P.5.1**. Generate the signals according to the timing diagram offered below as a support.



```

module dec_2x4 (
    output reg [1:0] s,
    output reg e,
    output [3:0] o
);

```

```
// Testbench instantiation
dec_2x4 DUT ( .s(s), .e(e), .o(o) );
// Selection signal generation
initial begin
s = 2'h0;
# 20 s = 2'h2;
# 20 s = 2'h1;
# 20 s = 2'h3;
# 20 s = 2'h0;
# 20 s = 2'h1;
# 20 s = 2'h3;
# 20 s = 2'h2;
# 20 s = 2'h1;
# 20 s = 2'h0;
end
// Enable signal generation
initial begin
e = 1'b1;
# 20 e = 1'b0;
# 20 e = 1'b1;
# 40 e = 1'b0;
# 20 e = 1'b1;
# 60 e = 1'b0;
# 20 e = 1'b1;
end
endmodule
```

**P.5.3.** Design, using Verilog language, a **parameterized module** for the register depicted in the initial architecture, having an 8-bit input and output, respectively the **load**, **clear**, **clock**, and **reset** signals on 1 bit.

**Solution:**

```

module rgst # (
parameter w = 8,
parameter iv = {w{1'b0}}
)(
input clk, rst_b, clr, ld,
input [w-1:0] d,
output reg [w-1:0] q
);
always @ ( posedge clk, negedge rst_b )
begin
if (! rst_b || clr)
q <= iv;
else if ( ld )
q <= d;
end
endmodule

```

**P.5.4.** Construct a parameterized 4-to-1 multiplexer, called ***mux\_2s***. The module will be parameterizable by its width, having the following interface:

```

module mux_2s #(
    parameter w = 4
)(
    input [w-1:0] d0 , d1 , d2 , d3 ,
    input [1:0] s ,
    output [w-1:0] o
);

```

**Solution:**

```
module mux_2s # (  
    parameter k = 8  
)(  
    input [1:0] s,  
    input [k-1:0] d0, d1, d2, d3,  
    output [w-1:0] o  
);  
assign o = s[1] ? (s[0] ? d3 : d2) : (s[0] ? d1 : d0);  
endmodule
```

**Alternative:**

```
module mux_2s # (  
    parameter k = 8 )(  
    input [1:0] s,  
    input [k-1:0] d0, d1, d2, d3,  
    output reg [w-1:0] o );  
always @ (*) begin  
    if (s==2'd3)  
        o = d3;  
    else if (s==2'd2)  
        o = d2;  
    else if (s==2'd1)  
        o = d1;  
    else o = d0;  
end  
endmodule
```

**P.5.5.** Design the Register File named *reg\_fl* by instantiating the *dec\_2x4* module, the *rgst* components, and the *mux\_2s* unit, accordantly.

**Solution:**

```

module reg_fl (
    input [7:0] wr_data,
    input [1:0] wr_addr, rd_addr,
    input wr_e, clk, rst_b,
    output [7:0] rd_data
);
    wire [3:0] w;
    wire [7:0] q0, q1, q2, q3;

    // Decoder Instantiation
    dec_2x4 decoder ( .s(wr_addr), .e(wr_e), .o(w) );

    // Registers Instantiation
    rgst # ( .w(8) ) register1 ( .d(wr_data), .ld(w[0]),
        .clk(clk), .rst_b(rst_b), .clr(1'b0), .q(q0) );
    rgst # ( .w(8) ) register2 ( .d(wr_data), .ld(w[1]),
        .clk(clk), .rst_b(rst_b), .clr(1'b0), .q(q1) );
    rgst # ( .w(8) ) register3 ( .d(wr_data), .ld(w[2]),
        .clk(clk), .rst_b(rst_b), .clr(1'b0), .q(q2) );
    rgst # ( .w(8) ) register4 ( .d(wr_data), .ld(w[3]),
        .clk(clk), .rst_b(rst_b), .clr(1'b0), .q(q3) );

    // Multiplexer Instantiation
    mux # ( .k(8) ) multiplexer ( .s(rd_addr), .d0(q0),
        .d1(q1), .d2(q2), .d3(q3), .o(rd_data) );

endmodule

```