 


Week 8 CA – Error Detection Architectures

Built-In Self-Test Architectures

P.8.1 Design a type ***D flip-flop*** with an additional asynchronous set line, as described in the given architecture:



- Implement, using Verilog language, the ***dff_ar*** module attached to the given design.
- Write a testbench that verifies the functionality of the ***dff_ar*** module by using the non-exhaustive checking procedure.

```
// Solution a):  
  
module dff_ar (  
    input d, rst_b, set_b, clk,  
    output reg q  
);  
  
always @(posedge clk, negedge rst_b) begin  
    if (set_b==0)  
        q <= 1'b1;  
    else  
        if (rst_b==0)  
            q <= 1'b0;  
        else q <= d;  
    end  
endmodule  
  
// Solution b):  
  
module dff_ar_tb (  
    output reg d, rst_b, set_b, clk,  
    output q  
);  
  
initial begin  
    clk=1'b0;  
    repeat (4) #20 clk = ~clk;  
end  
  
initial begin  
    rst_b=1'b0;  
    #5 rst_b = 1'b1;  
end
```

```
initial begin
set_b=1'b1;
#60 set_b = 1'b0;
#10 set_b=1'b1;
end

initial begin
d=1'b0;
#40 d = 1'b1;
#20 d = 1'b0;
end

endmodule
```


P.8.2. Design a 4-bit serial right shift register with feedback, the outputs of which are generated in the given truth table as support. This requires the following aspects:

- Fill in the truth table with the missing 4-bit vectors and determine the periodicity of the output sequence.
- Implement, using Verilog language, the 4-rank Linear Feedback Shift Register (LFSR) unit, using instances of the dff_ar module designed in **P.9.1**.

The solution for a) is provided in the laboratory material.

```
module LFSR (  
    input clk, rst_b, set_b,  
    output [3:0] q  
);  
    // Instantiation  
    dff_ar dff0 ( .d(q[3]),  
                  .clk(clk),  
                  .rst_b (1'b1),  
                  .set_b (set_b),  
                  .q (q[0]) );  
    dff_ar dff1 ( .d(q[3] ^ q[0]),  
                  .clk(clk),  
                  .rst_b (1'b1),  
                  .set_b (set_b),  
                  .q (q[1]) );  
    dff_ar dff2 ( .d(q[1]),  
                  .clk(clk),  
                  .rst_b (1'b1),  
                  .set_b (set_b),  
                  .q (q[2]) );  
    dff_ar dff3 ( .d(q[2]),  
                  .clk(clk),  
                  .rst_b (1'b1),  
                  .set_b (set_b),  
                  .q (q[3]) );  
endmodule
```

 P.8.3. Implement a 4-bit Single Input Signature Register (**SISR**) using Verilog language, as shown below.



```

module SISR (
    input i, clk, rst_b, set_b,
    output [3:0] q
);
    // Instantiation
    dff_ar dff0 ( .d(i ^ q[3]),
                  .clk(clk),
                  .rst_b (rst_b),
                  .set_b (1'b1),
                  .q (q[0]) );
    dff_ar dff1 ( .d(q[3] ^ q[0]),
                  .clk(clk),
                  .rst_b (rst_b),
                  .set_b (1'b1),
                  .q (q[1]) );

```


```

dff_ar dff2 ( .d(q[1]),
              .clk(clk),
              .rst_b (rst_b),
              .set_b (1'b1),
              .q (q[2]) );
dff_ar dff3 ( .d(q[2]),
              .clk(clk),
              .rst_b (rst_b),
              .set_b (1'b1),
              .q (q[3]) );
endmodule

```

P.8.4. Design, using Verilog language, a Built-In Self-Test (**BIST**) architecture that uses the following components in its structure:

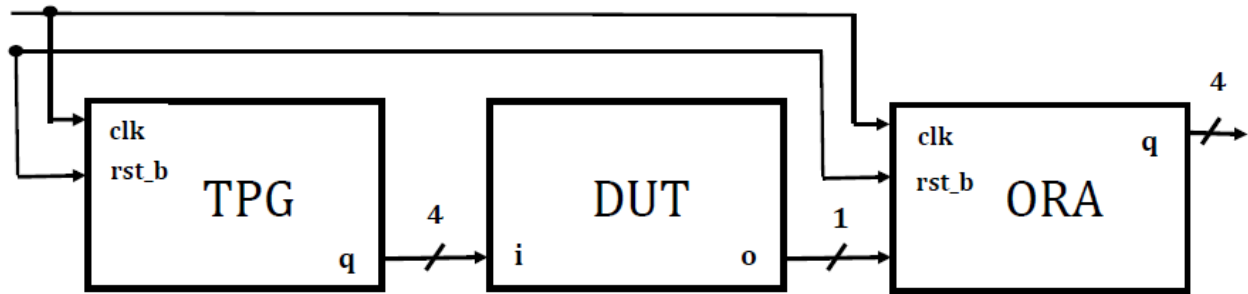- The 4-bit **LFSR** implemented in **E10.2** will replace the TPG unit.
- The **DUT** will be replaced by a combinational circuit that provides a bit of **1** if the input *i* of the block is a multiple of 3, and **0** otherwise.
- The 4-bit **SISR** will replace the **ORA** unit in the given diagram.



```

module BIST (
    input clk, rst_b, set_b,
    output [3:0] q
);
    wire [3:0] w1;
    wire w2;
    // Instantiation
    LFSR TPG ( .clk(clk),
                .rst_b (1'b1),
                .set_b (set_b),
                .q (w1)
    );
    MUL_3 DUT ( .i (w1),
                .o (w2)
    );
    SISR ORA ( .clk(clk),
                .rst_b (rst_b),
                .set_b (1'b1),
                .i(w2),
                .q (q)
    );
endmodule

```